THE AMERICAN COLLEGE, MADURAI

(An Autonomous Institution Affiliated to Madurai Kamaraj University) Re-accredited (2^{nd} Cycle) by NAAC with Grade "A", CGPA - 3.46 on a 4-point scale

Backlog Arrear Examination, March 2021

Course: MCA 4403/ 4423 Time: 3 Hrs

Title : Digital Principles and Computer Organization Max : 75 marks

Answer any FIVE questions:

 $5 \times 15 = 75$

- 1. Explain any four number systems and codes along with its uses.
- 2. Explain the POS method with a suitable example.
- 3. Explain the 1-to-16 De-multiplexer logic circuit.
- 4. Explain with the block diagram basic computer organization
- 5. Design and simplify a BCD to excess-3 logic circuit.
- 6. What is a Karnaugh map? Justify how it yields maximum simplification with suitable examples.
- 7. Comment on the primary memory.