

## THE AMERICAN COLLEGE, MADURAI

(An Autonomous Institution Affiliated to Madurai Kamaraj University) Re-accredited (2<sup>nd</sup> Cycle) by NAAC with Grade "A", CGPA – 3.46 on a 4-point scale

## Backlog Arrear Examination, March 2021

Course code: PHS 1563 Time: 3 Hrs

Course Title: Digital Electronics and its application Marks: 75

## **PART-A**

## Answer any five of the following questions.

5x15=75

- 1. Discuss the different types of logic gate with its truth tables.
- 2. (i) Convert (64)<sub>10</sub> to binary.
  - (ii) Convert the octal number (88)<sub>8</sub> to decimal.
  - (iii) Convert the binary number (10110110) to hexadecimal.
- 3. State and verify De Morgan's law.
- 4. Explain JK flip flop with its circuit diagram and truth table.
- 5. With the help of block diagram and waveform explain the serial in serial out shift registers.
- 6. What is Multiplexers? Explain the 4-to-1 multiplexer.
- 7. With a neat diagram and output waveform, explain the operation of asynchronous counter.

\*